

CSE 141L  
SPRING, 2017

# VERILOG MODULES

May 12, 2017

Author: Chenxu Jiang  
PID: A92114155  
Author: Dingcheng Hu  
PID: A92090168

## 1 Introduction

In this lab, we build verilog modules for our CPU, in logic level. We build the following modules:

**ALU** supports addition/subtraction, 1-bit shifting, and branching decision.

**Register File** contains 3 sub-module, Accumulator Register Regular Register and Single-Bit Register.

**Data Memory** is 256 in depth and 8-bit in width, supports reads and writing to an memory address.

**Instruction Fetch** that contains Program Counter (its increment, branching and halting logic), Instruction Memory that stores read-only instruction memory and Look-up Table that stores branching address.

## 2 ISA Summarization

There are following types of operations supported:

### Data Type:

- Load from Memory Address to Register
- Store from Register to Memory Address.
- Copy Data in one Register to another Register.

### Arithmetic Type:

- Addition/Subtraction of 2 Registers with/without Stored Overflow Bit.
- Right Shifting Logically/Arithmetically/use stored Overflow Bit as shift-in.
- Left Shifting that always use Overflow Bit as shift-in.

### Miscellaneous:

- Zero Specified Register.
- Decrementing Specified Register by 1.
- Add one Register 1 to Register 2 only if Register 3 is not negative.
- Flip stored Flip-bit if specified register is negative.
- Add 1 to Register 1 if the upper-4-bit of Register 2 and 3 matches.
- Add flip bit xor flag bit to specified register.

### Branching:

- Branch if specified register is not 0.
- Branch if upper-4-bit of specified register is not 0.
- Branch if the register not equal to 31.

## 3 ALU Operations

ALU need to support all Arithmetic Type, Miscellaneous and Branching Instruction.

### Arithmetic Type:

- Addition/Subtraction of 2 Registers with/without Stored Overflow Bit.
  - add1, add4, add5, addf0, addf4, sub1, sub3, sub4, sub5, subf2, sub25, add25, subf25
- Right Shifting Logically/Arithmetically/use stored Overflow Bit as shift-in.
  - srl, sra, srf, srl4, sra5, srf5
- Left Shifting that always use Overflow Bit as shift-in.
  - slf0, slf1, slf2

### Miscellaneous:

- Zero Specified Register.
  - zero0, zero2, zero3, zero4
- Decrementing Specified Register by 1.
  - dec1

Add one Register 1 to Register 2 only if Register 3 is not negative.

- `add3_n2, add4_n2`

Flip stored Flip-bit if specified register is negative.

- `atos_2`

Add 1 to Register 1 if the upper-4-bit of Register 2 and 3 matches.

- `add0c25`

Add flip bit xor flag bit to specified register. - `inc_af0`

### Branching:

Branch if specified register is not 0.

- `bnzr`

Branch if upper-4-bit of specified register is not 0.


- `bnuzr`

Branch if the register not equal to 31.


- `b1ne31`

## 4 Verilog Modules

### 4.1 Hierarchy Tree

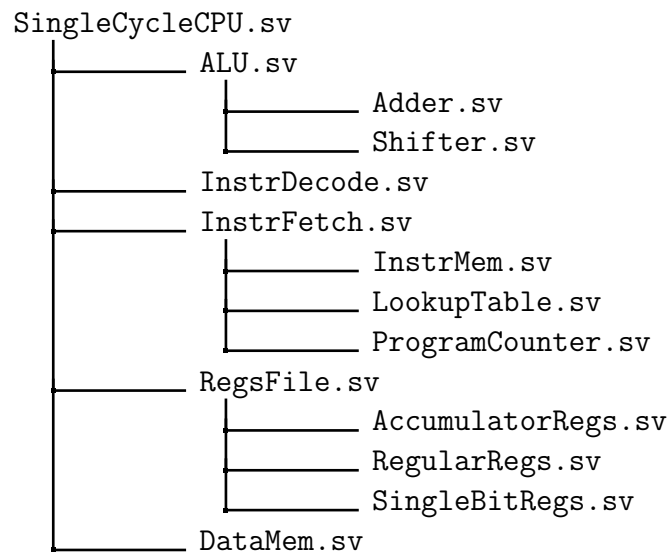

## 4.2 Schematics

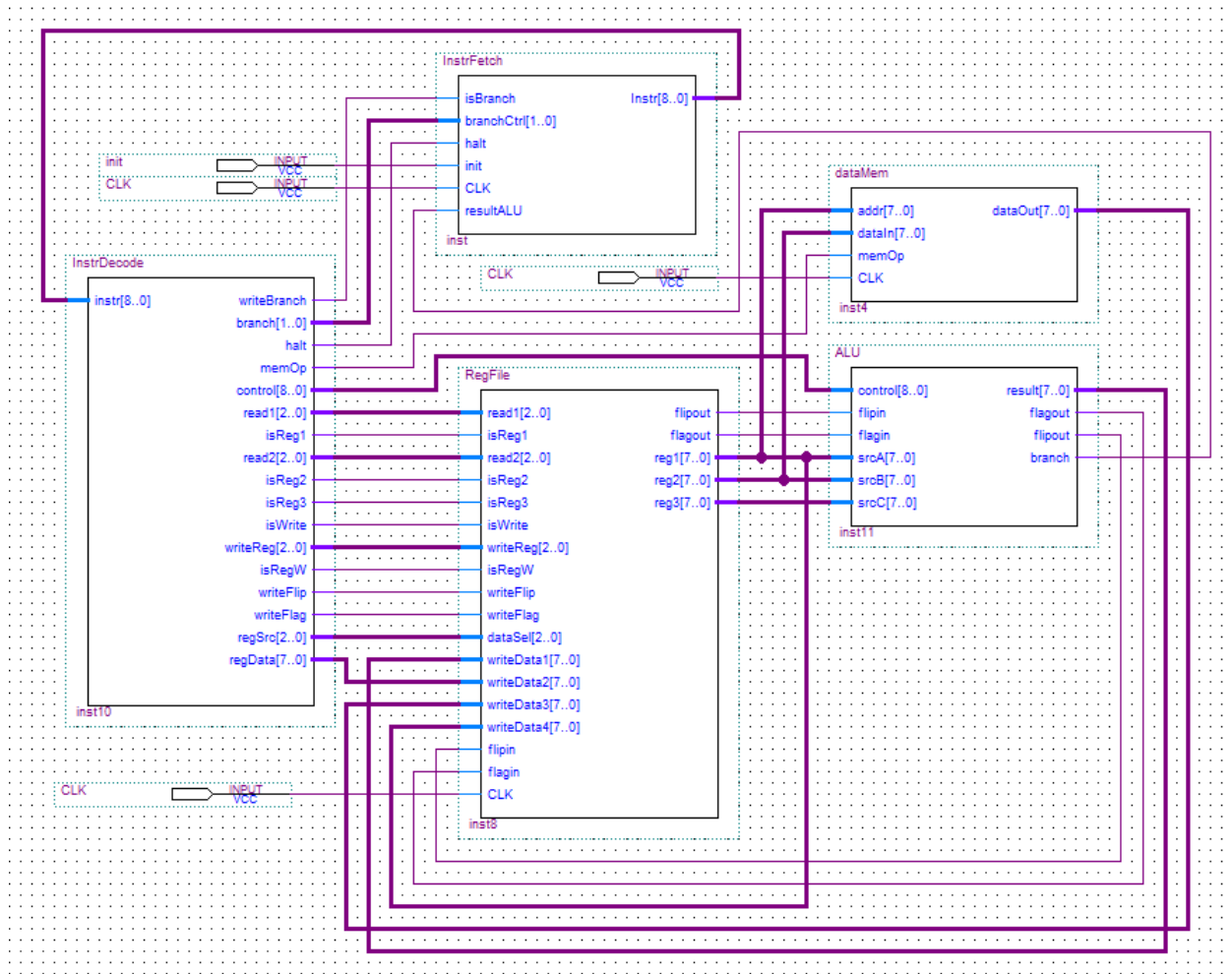

## 5 Time Diagram

### 5.1 ALU Test

Time Diagram

5.1 ALU Test

Name	20ns	40ns	60ns	80ns	100ns	120ns	140ns	160ns	180ns	200ns	220ns	240ns							
result[7:0]	hxx	h94	h00	hF1	hFF	i01	hC0	h40	h80	h03	hAA	h00	h01	h00	h01	h00	h01	h00	h01
flagout																			
branch																			
control[3:0]	hxxx	h0XX	h0XX	h0XX	h0XX	h1XX	hxxx	hxxx	hxxx	hxxx	hxxx	hxxx	hxxx	h0xx	hxxx			h0XX	
flagin																			
flipIn																			
srcA[7:0]	hxx	h3F	hFF		h00		h81	h01	h81	hxx	hFF	h00	h40	h0x	h1X	hFF	h1F		hFF
srcB[7:0]	hxx	h55	h00	h0E	h00														
srcC[7:0]							hxx				hAA	h80	hAA						

#1 Add 2 Number Without Overflow:  
srcA(00111111) + srcB(01010101) + flagin(0) = flagout(0) + result(10010100)

#2 Add 2 Number With Overflow and Carry In + test ignore Flip bit:  
srcA(11111111) + srcB(00000000) + flagin(1) = flagout(1) + result(00000000)

#3 Sub 2 Number With no borrow + test ignore Flag bit:  
srcA(11111111) - srcB(00001110) (flagin(1)) = flagout(0) + result(11110001)

#4 Sub 2 Number With borrow:  
srcA(00000000) - srcB(00000000) - flagin(1) = flagout(1) + result(11111111)

#5 Sub 2 Number With borrow:  
srcA(00000000) - srcB(11111111) - flagin(0) = flagout(1) + result(00000001)

#6 Sub 2 Number ignore srcB, use 1 instead:  
srcA(00000000) - srcB(11111111) (1) - flagin(0) = flagout(0) + result(00000001)

#7 srl test right shift arithmetically  
(0) srcA(10000001) >> 1 = result(11000000) (1)

#8 srl test right shift logically  
(1) srcA(10000001) >> 1 = result(01000000) (1)

#9 srf test right shift use overflow bit as shift-in  
(1) srcA(00000001) >> 1 = result(10000000) (1)

#10 slf test left shift use overflow bit as shift-in  
srcA(10000001) (1) << 1 = (1) result(00000011)

#11 test never branch  
srcA = xxxxxxxx, never branch control set, branch = 0;

#12 test branch when srcA != 0  
srcA = 00000000, branch = 0;

#13 test branch when srcA != 0  
srcA = 01000000, branch = 1;

#14 test branch when upper 4 srcA != 0  
srcA = 0000xxxx, branch = 0;

#15 test branch when upper 4 srcA != 0  
srcA = 0001xxxx, branch = 1;

#16 test branch when srcA != 31  
srcA = 11111111, branch = 1;

#17 test branch when srcA != 31  
srcA = 00011111, branch = 0;

#18 test result = srcA + (srcB < 0? 0: srcC)  
srcA = 00000000, srcB = 00000000, srcC = 10101010; result = 10101010

#19 test result = srcA + (srcB < 0? 0: srcC)  
srcA = 00000000, srcB = 10000000, srcC = 10101010; result = 00000000

#20 test result = srcA + (upper4 match srcB, srcC? 1: 0)  
srcA = 00000000, srcB = 10100000, srcC = 10101111; result = 00000001

#21 test result = srcA + (upper4 match srcB, srcC? 1: 0)  
srcA = 00000000, srcB = 10111111, srcC = 10101111; result = 00000000

#22 test result = srcA + flip ^ flag  
srcA = 00000000, flip = 0, flag = 1; result = 00000001

#23 test result = srcA + flip ^ flag  
srcA = 00000000, flip = 0, flag = 0; result = 00000000

#23 test result = srcA + flip ^ flag  
srcA = 00000000, flip = 1, flag = 1; result = 00000000

## 5.2 Register File Test

#1 test write to and read from accumulator registers  
 read1 = 000, isReg1 = 0, writeReg = 000, isRegW = 0, writeData = 01101001  
 correctly write to \$acc0

#2 test read from regular register of the same index  
 read1 = 000, isReg1 = 0  
 correctly write to \$acc0


#3 test write to and read from regular registers  
 read2 = 001, isReg2 = 1, writeReg = 001, isRegW = 1, writeData = 11110000  
 correctly write to \$t1

#4 test accumulative register not contaminate  
 isReg2 = 0  
 \$acc1 still undefined

#5 test disabled  
 write new value does not write into  
 correctly write to \$t1

#6 test write to \$acc0 again  
 \$acc0 now write to 11111111
 
#7 test write to and read from acc5  
 read2 now read from acc5, it is set to new value  
 acc5 always output acc5, it is also set



### 5.3 Instruction Fetch Test

Instruction Memory is set to

```
000000000
000000001
000000010
000000011
000000100
000000101
000000110
...
```

to match with PC

Look up table branch is

```
000000000
000000011
100000000
000000001
```

#1 test initialize  
instruction set to 00000000

#2 test let clock run  
instruction set to 00000001

#3 test let clock run  
instruction set to 00000010


#4 test let clock run  
instruction set to 00000011

#5 test let clock run  
instruction set to 00000100

#6 test ALU judge branch fail  
instruction set to 00000101

#7 test ALU judge branch successful  
instruction set to 00000011
 
#8 test halt  
instruction remain at 00000011



## 6 Non-Arithmetic Instruction in ALU

We use ALU for determining branching. We use 3 branching and the determination is paralleled with adder and shifter. Therefore, for time's sake there is no difference. But more gates are used to judge if branch or not.

## 7 Easier Instruction Fetch

We think our Instruction Fetch is already easy enough. It can be made without branching address stored in lookup table. But without lookup table the branching distance would be limited to only  $\pm 8$  instructions, which is not enough.

## 8 Easier ALU Design

Our ALU does too much jobs, since there are lots of instructions specifically made up for the 3 program, to reduce instruction count. If we don't need to reduce instruction count, then the logic in ALU can be limited to adder and shifter, and become easier.

## 9 Easier Register File

Our register file is very complicated, since we divide it into 2 parts, Accumulator Registers and Regular Registers. It is divided, since we have only 9-bit instruction and we manage to give register 2-bit. Therefore, we came to the idea of dividing register. Regular register can be used as argument, and accumulator register can be used as accumulator, and is included in the instruction name. Division of register file is like putting a mux manually between the 2 register files. If we have more bits for instruction code, then we will not need the division. And our register file can be easier.

## 10 Most Complex Instruction ALU

`add3_n2`, `add4_n2`, `add0c25`, `inc_af0` are 4 most complex instructions for ALU. They are the only 4 instructions that need ALU to preprocess the input to adder. The other instructions have values directly go to adder or shifter.

## 11 Additional Function of ALU

No. The design can only execute instructions that it is made for.